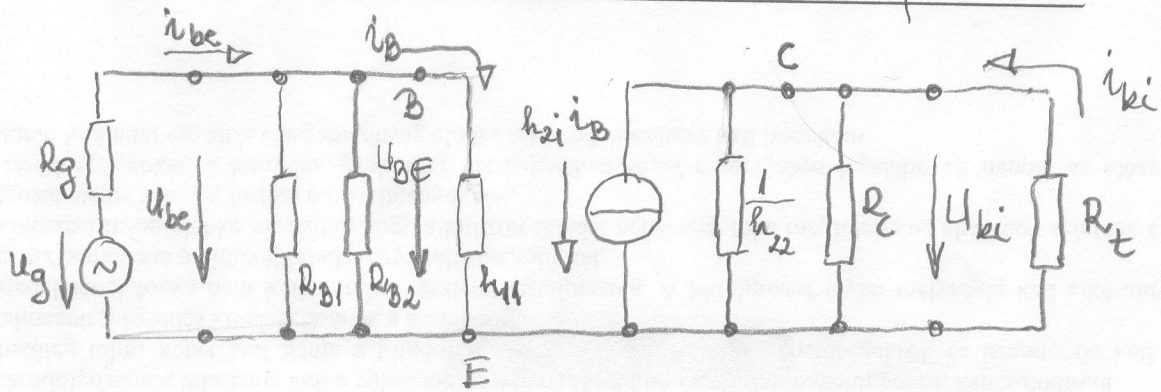


KE enélőforrót mőltakozó áramú jellemzői




$$R_{be} = R_{b1} \times R_{b2} \times h_{ie}$$

$$R_{ki} = \frac{1}{h_{22}} \times R_c$$

$$A_u = -\frac{h_{21}}{h_{11}} \cdot \left(\frac{1}{h_{22}} \times R_c \times R_t \right) = -S(R_{ki} \times R_t) ; S = \frac{h_{21}}{h_{11}}$$

$$A_i = -A_u \frac{R_{be}}{R_t}$$

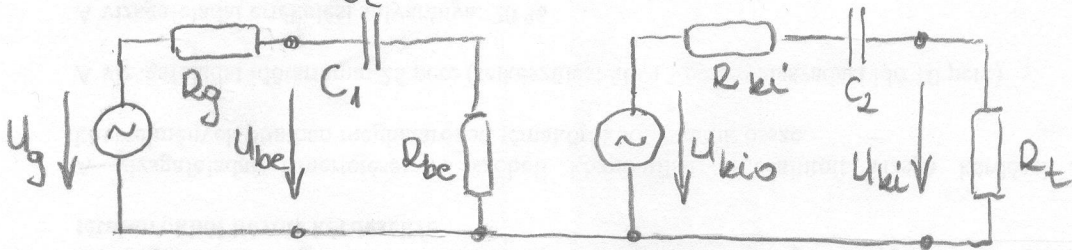


$$f_{a1} = \frac{1}{2\pi C_1 (R_{be} + R_g)}$$

$$f_{a2} = \frac{1}{2\pi C_2 (R_{ki} + R_t)}$$

$$f_{aE} = \frac{1}{2\pi C_E R_E} \cdot \frac{A_u}{A_{uv}}$$

$$A_{uv} = -h_{21} \frac{R_c \times R_t}{h_{11} + (1 + h_{21}) \cdot R_E}$$

$$f_a = \max(f_{a1}, f_{a2}, f_{aE})$$

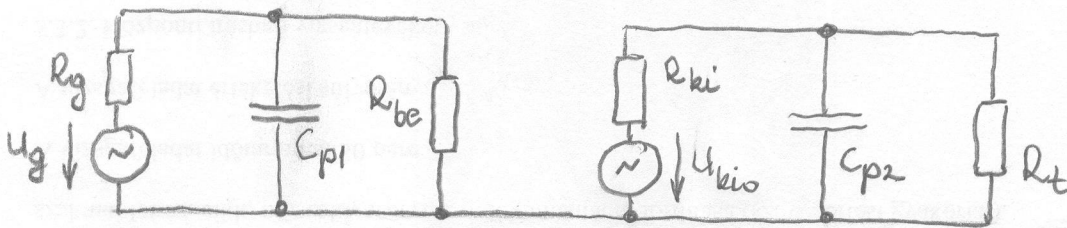

$$C_{pi} = C_{BE} + (1 - A_u) \cdot C_{CB} + C_{kz1}$$

$$f_{f1} = \frac{1}{2\pi \cdot C_{pi} (R_g \times R_{be})}$$

$$C_{p2} = C_{CE} + C_{kzki}$$

$$f_{f2} = \frac{1}{2\pi \cdot C_{p2} (R_{ki} \times R_t)}$$

$$f_f = \min(f_{f1}, f_{f2})$$

$$B = f_f - f_a$$

Közepes frekvencia

Alacsony frekvencia

Magas frekvencia